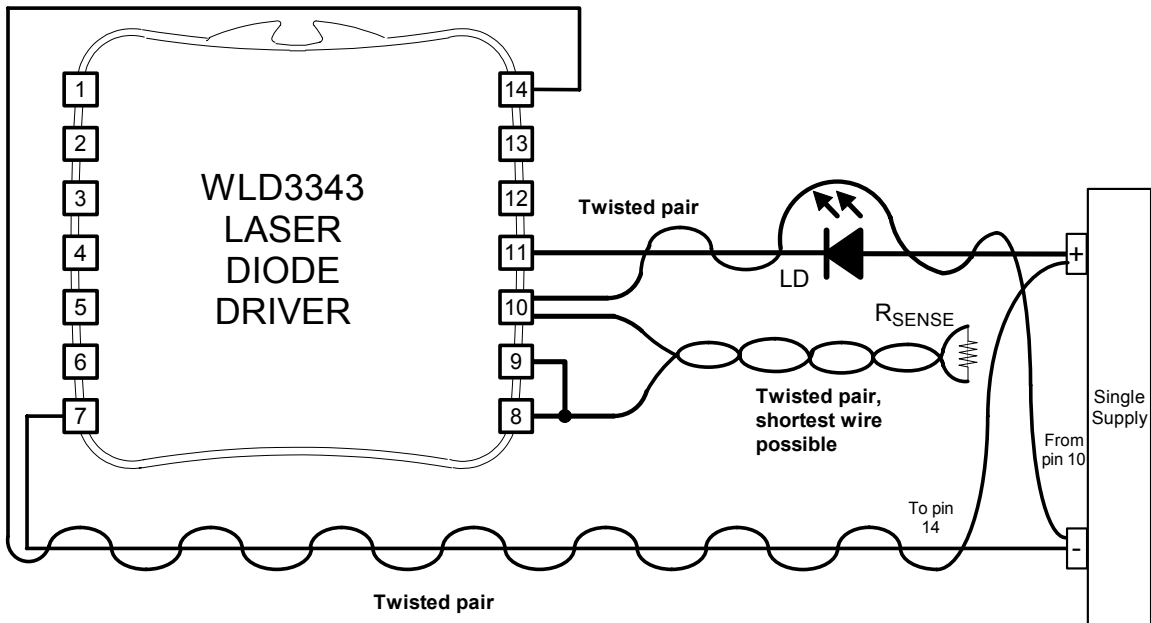


# Power Wiring Diagram to minimize noise with WLD3343



**Refer to Data Sheet for complete circuit**